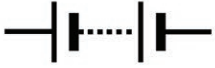

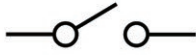







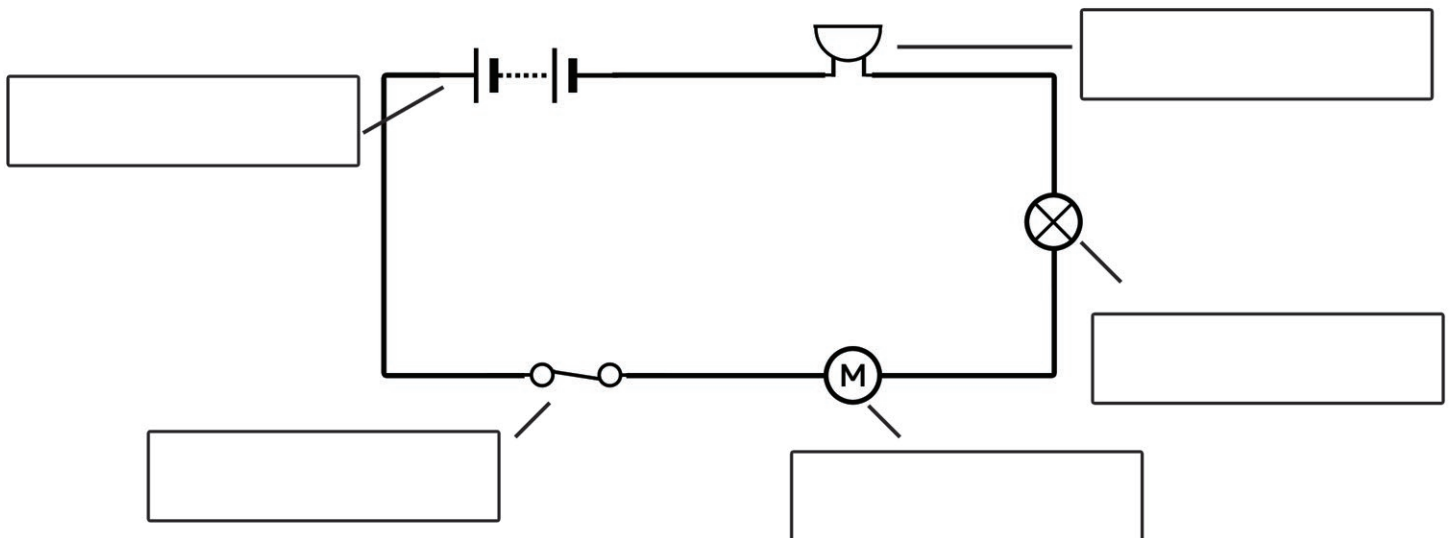


# Electric Circuits

Electricity flows in a circuit from the negative pole of the battery to its positive pole. The flow of electricity creates an electric current. There is a symbol to represent each component in an electrical circuit.

|  |  |  |  |  |
|--|--|--|--|--|
| <br>battery | <br>closed switch | <br>open switch | <br>cell  | <br>voltmeter |
| <br>buzzer  | <br>lamp          | <br>lamp        | <br>motor | <br>wire      |

Label the circuit below.



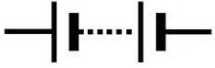

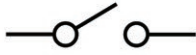







Complete the sentences.

The electric current leaves the \_\_\_\_\_ and passes through the \_\_\_\_\_.

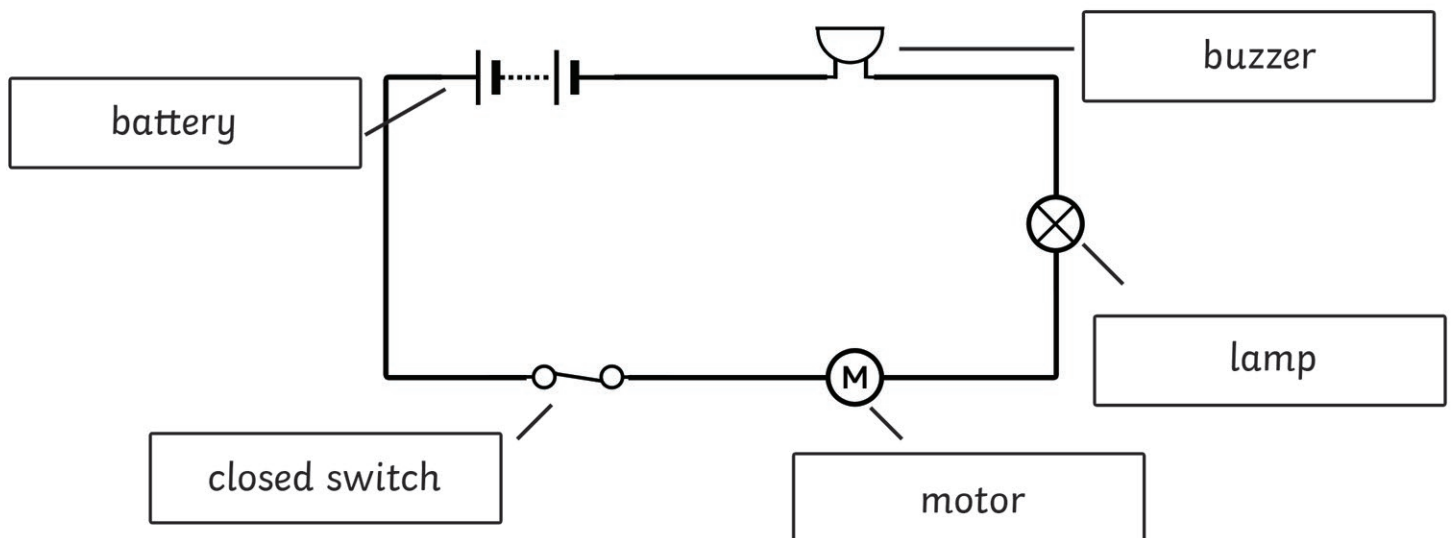
It then travels through the \_\_\_\_\_, next through the \_\_\_\_\_ and finally through the \_\_\_\_\_ before returning to the battery.

# Electric Circuits - Answers

Electricity flows in a circuit from the negative pole of the battery to its positive pole. The flow of electricity creates an electric current. There is a symbol to represent each component in an electrical circuit.

|  |  |  |  |  |
|--|--|--|--|--|
| <br>battery | <br>closed switch | <br>open switch | <br>cell  | <br>voltmeter |
| <br>buzzer  | <br>lamp          | <br>lamp        | <br>motor | <br>wire      |

Label the circuit below.



Complete the sentences.

The electric current leaves the battery and passes through the closed switch.

It then travels through the motor, next through the lamp and finally through the buzzer before returning to the battery.